

Name: Farhan Akbor Khan

ID: 20301230


Section: 07

Lab Test - 06

CSE460 (Summer-23)


Date: 15 - 08 -2023

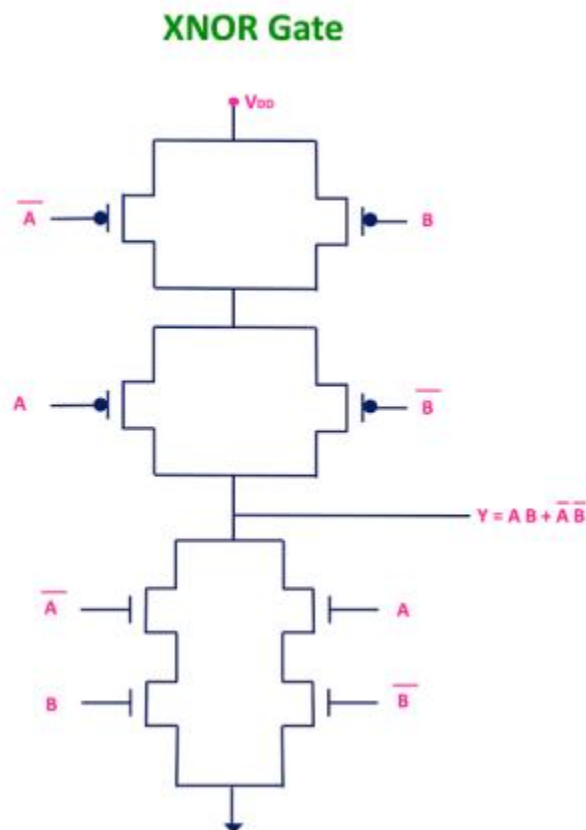Question: Implement the layout of the following circuit using Microwind. You are supposed to design it manually (not using verilog) and must show that there are no DRC errors. Also, you have to show the waveforms of the circuit you've generated.





Answer:

Stick Diagram For above X-Nor Gate

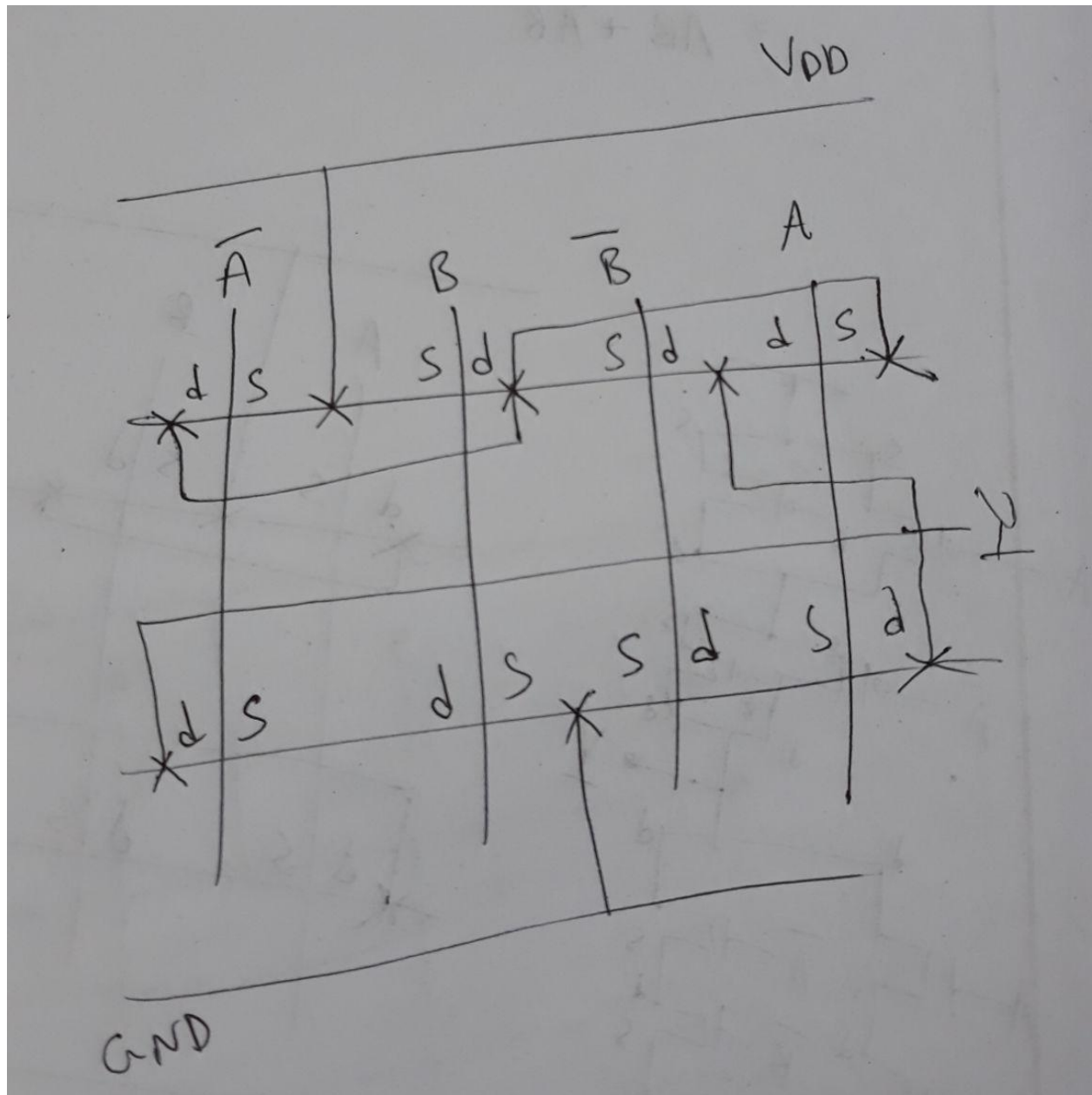

Layout

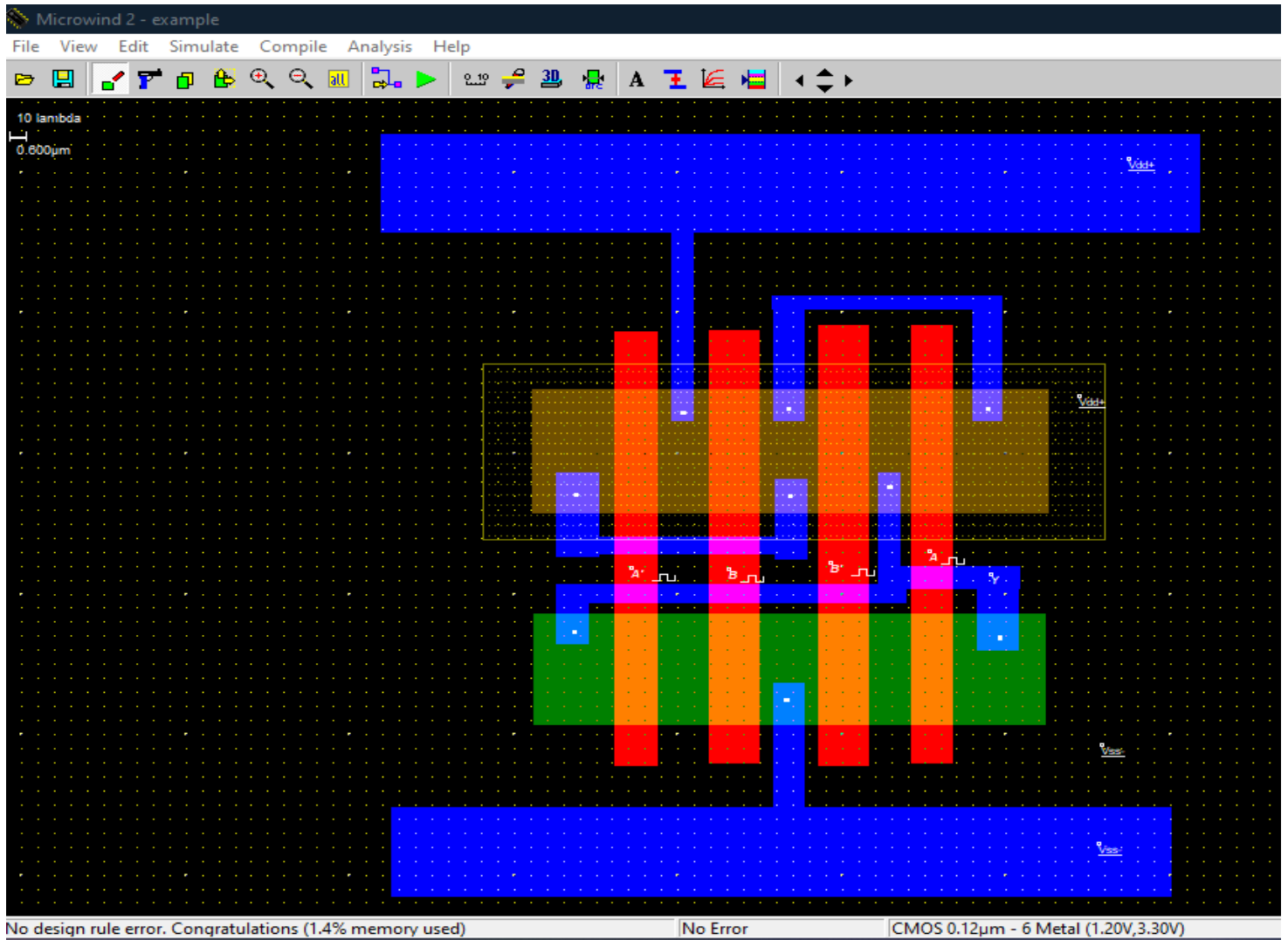

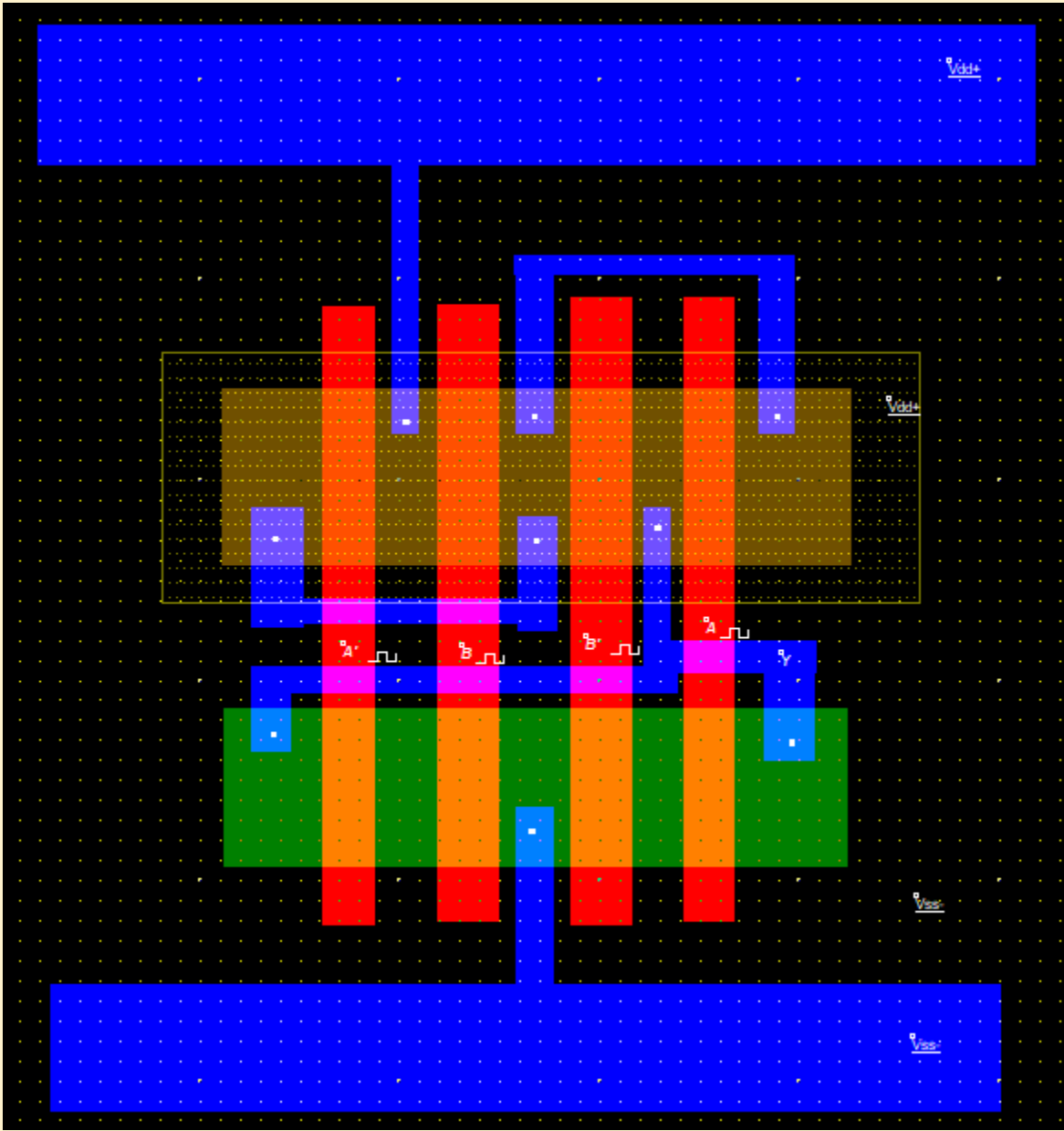

Waveform

