

BRAC UNIVERSITY
VLSI DESIGN
CSE460L (Summer 2023)
SECTION: 07
Time: 20 minutes

Name: _____


Student ID: _____

Problem

[10]

You have to design a D latch in DSCH2 using a 2 to 1 Multiplexer as shown in the following figure. D and Q are the latch's data input and output, respectively. The MUX's selector pin is a clock signal (CLK). You are not allowed to use gates (made using CMOS) other than **NAND** and **NOT** to implement the MUX.

 [Hints: You may use the expression $\overline{(\overline{sA}) \cdot (\overline{sB})}$ to implement the MUX using CMOS NAND and NOT logic only, with A and B being the two inputs to the MUX and s being the selection pin.]



Note: You may use blocks/sub-circuits made using CMOS technology but **cannot use readily available logic gates**. In a timing diagram, show the simulated input and output waveforms. You may synchronize the inputs with clocks.

Name: Farhan Akbor Khan

ID: 20301230

Section: 07

Lab Assignment: 01

CSE460L

