

CSE460L: VLSI Design
Lab Assignment 2 (Summer 23)
Section: 07
Time: 30 mins

Problem:

Consider the boolean logic function below:

$$F = \overline{A + (\overline{B} \cdot (C + \overline{D}))}$$

- (a) Compile a **structural** Verilog Code for the function using Quartus.
- (b) Prepare a vector waveform file (.vwf) using clock signals of appropriate periods required to produce all 16 combinations of the input variables and generate the simulation report.
- (c) Compile a **behavioral** Verilog Code for the function using Quartus.
- (d) Prepare a vector waveform file (.vwf) using clock signals of appropriate periods required to produce all 16 combinations of the input variables and generate the simulation report.
- (e) Comment on whether both of the simulation reports are identical or not.

Farhan Akbor Khan


ID: 20301230

Section: 07

Lab02

CSE460
 
$$F = \overline{A + (\bar{B} (C + \bar{D}))}$$



a)

```
module LA2_T1_20301230(A,B,C,D,F);
```

```
  input A,B,C,D;
```

```
  output F;
```

```
  wire b,d,e,g;
```

```
  not(b,B);
```

```
  and (g, b, e);
```


```
  or (e, C, d);
```

```
  not (d, D);
```

```
  nor (F, A,g);
```

```
endmodule
```

b)

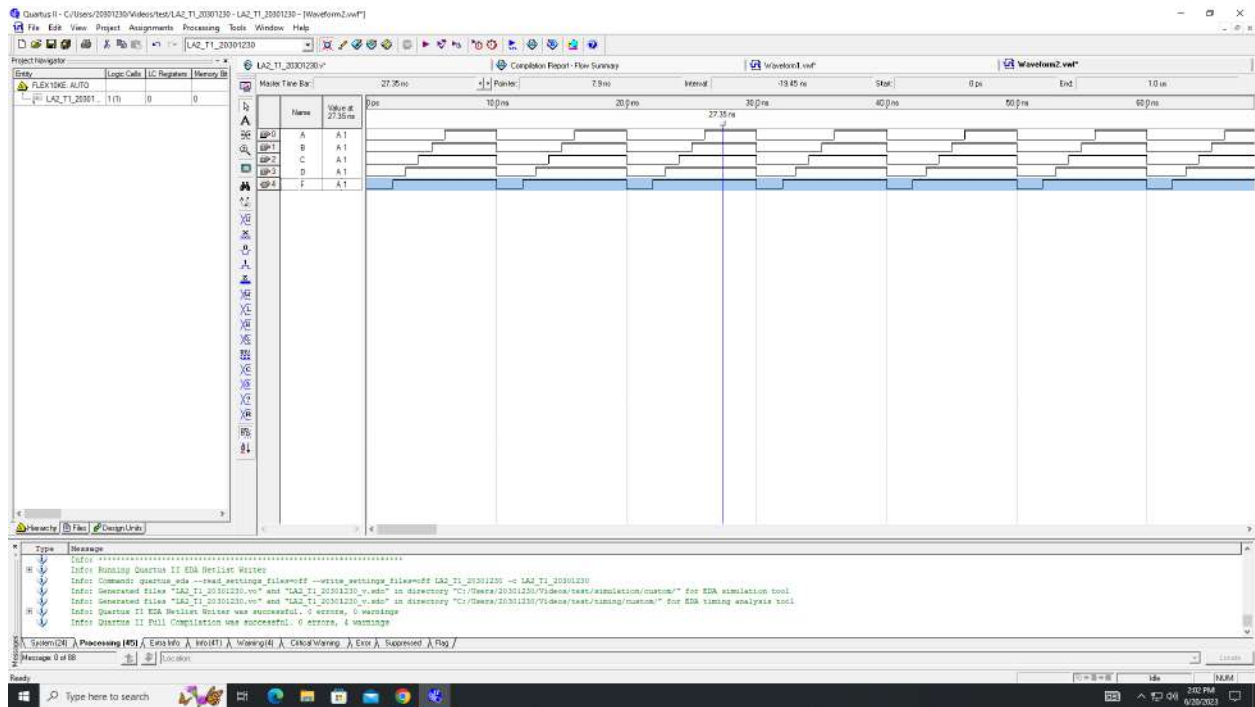

c)


```

module LA2_T1_20301230(A,B,C,D,F);
    input A,B,C,D;
    output F;
    wire B_sum;
    assign B_sum= C+ ~D;
    assign F= ~(A+(~(B) * B_sum));

endmodule

```

d)

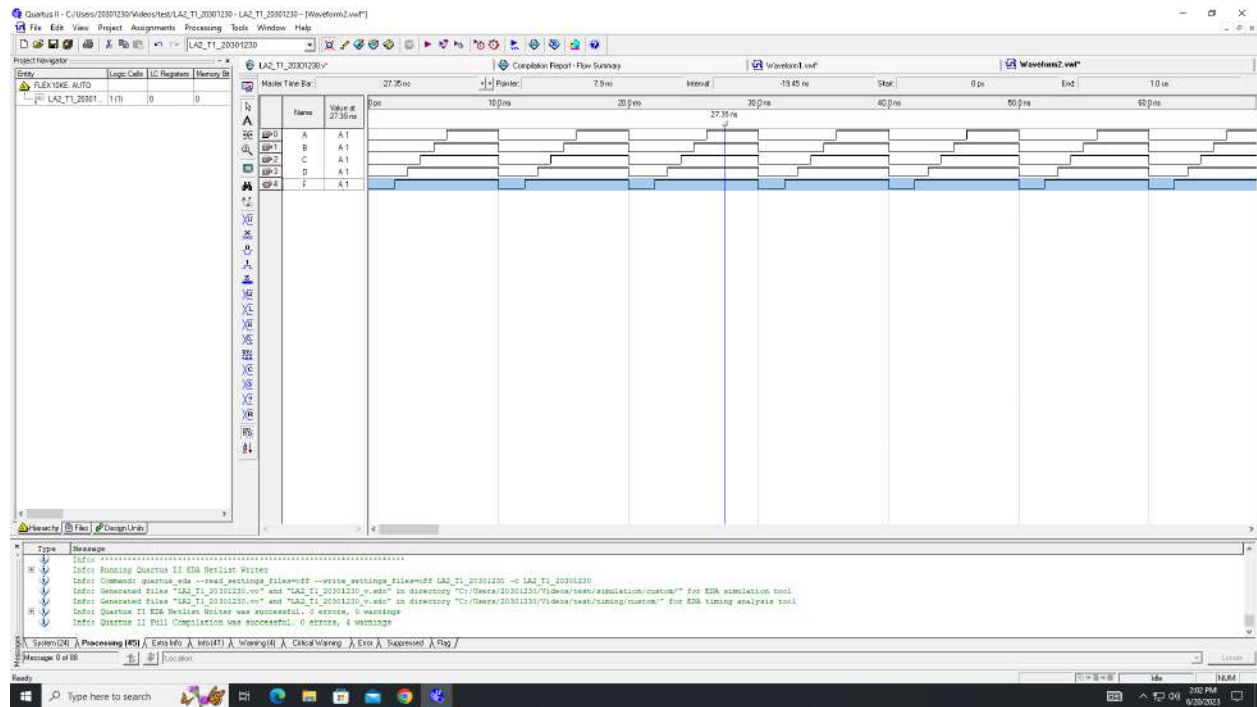

e)

Both are the same if the clock cycles are the same.